

Telangana State Council Higher Education

Notations :

- Options shown in **green** color and with  icon are correct.
- Options shown in **red** color and with  icon are incorrect.

Question Paper Name :	Electrical Engineering 1st Jun 2026 Shift 2
Subject Name :	Electrical Engineering
Creation Date :	2026-06-01 16:30:01
Duration :	120
Total Marks :	120
Display Marks:	Yes
Share Answer Key With Delivery Engine :	Yes
Actual Answer Key :	Yes
Change Font Color :	No
Change Background Color :	No
Change Theme :	No
Help Button :	No
Show Reports :	No
Show Progress Bar :	No

Electrical Engineering

Group Number :	1
Group Id :	10513148
Group Maximum Duration :	0
Group Minimum Duration :	120
Show Attended Group? :	No
Edit Attended Group? :	No
Break time :	0
Group Marks :	120

Mathematics

Section Id :	105131105
Section Number :	1
Section type :	Online

Mandatory or Optional :	Mandatory
Number of Questions :	10
Number of Questions to be attempted :	10
Section Marks :	10
Maximum Instruction Time :	0
Sub-Section Number :	1
Sub-Section Id :	105131105
Question Shuffling Allowed :	Yes

Question Number : 1 Question Id : 1051316121 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

If $A = \begin{bmatrix} 1 & 1 & 2 \\ 2 & 5 & 4 \\ 1 & 0 & 5 \end{bmatrix}$, then determinant of $(A^{2026} - 11A^{2025} - 9A^{2023}) =$

Options :

1. ✗ 9^{2026}
2. ✗ $(-31)^3 3^{2025}$
3. ✓ $(-31)^3 3^{4048}$
4. ✗ $(31)^4 3^{4048}$

Question Number : 2 Question Id : 1051316122 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

An Eigen value of the matrix $\begin{bmatrix} 1 & -1 & 2 \\ 0 & 1 & 0 \\ 1 & 2 & 1 \end{bmatrix}$ is 1. An eigen vector corresponding to it is

Options :

1. ✗ $\begin{bmatrix} 3 \\ 2 \\ 0 \end{bmatrix}$

2. ✖ $\begin{bmatrix} 4 \\ 2 \\ -1 \end{bmatrix}$

3. ✔ $\begin{bmatrix} -4 \\ 2 \\ 1 \end{bmatrix}$

4. ✖ $\begin{bmatrix} 3 \\ 2 \\ 1 \\ \frac{1}{2} \end{bmatrix}$

Question Number : 3 Question Id : 1051316123 Question Type : MCQ Option Shuffling : Yes
 Display Question Number : Yes
 Correct Marks : 1 Wrong Marks : 0

If $z = x^2y + e^{xy^2}$, then $\left(\frac{\partial^2 z}{\partial x^2} + \frac{\partial^2 z}{\partial x \partial y} \right)$ at $(1, 0)$ is

Options :

1. ✖ 0

2. ✖ 1

3. ✔ 2

4. ✖ -2

Question Number : 4 Question Id : 1051316124 Question Type : MCQ Option Shuffling : Yes
 Display Question Number : Yes
 Correct Marks : 1 Wrong Marks : 0

If $f(x) = x^3$, $0 \leq x \leq 4$, $f(x+4) = f(x) \forall x \in \mathbb{R}$ and the Fourier series of $f(x)$ is

$$f(x) = \sum_{n=0}^{\infty} \left(a_n \cos \frac{n\pi x}{2} + b_n \sin \frac{n\pi x}{2} \right), \text{ then } a_0 =$$

Options :

1. ✖ 8
2. ✖ 32
3. ✔ 16
4. ✖ 24

Question Number : 5 Question Id : 1051316125 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The particular integral of $(D^4 - D^3 - 9D^2 - 11D - 4)y = e^{-x}$, $D = \frac{d}{dx}$ is

Options :

1. ✖ $-\frac{x^2 e^{-x}}{20}$
2. ✖ $-\frac{x e^{-x}}{15}$
3. ✔ $-\frac{x^3 e^{-x}}{30}$
4. ✖ $-\frac{e^{-x}}{10}$

Question Number : 6 Question Id : 1051316126 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The solution of $\frac{\partial^2 z}{\partial x^2} + z = 0$, satisfying $z(0, y) = e^y$, $\left(\frac{\partial z}{\partial x} \right)_{x=0} = 1$ is $z(x, y) =$

Options :

1. ✖ $e^y \sin x + \cos x$
2. ✖ $\sin x + e^y e^x \cos x$
3. ✔ $e^y \cos x + \sin x$
4. ✖ $e^y \cos x + y \sin x$

Question Number : 7 Question Id : 1051316127 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Let $r = \min\{\alpha, \beta, \gamma\}$, $R = \max\{\alpha, \beta, \gamma\}$, $f(z) = \frac{z}{(z-\alpha)(z-\beta)(z-\gamma)}$. $I_1 = \int_{C_1} f(z) dz$ and

$I_2 = \int_{C_2} f(z) dz$, where $C_1 : |z| < r$ and $C_2 : |z| = R+1$, then $I_1 + I_2 =$

Options :

1. ✖ $2\pi i$
2. ✔ 0
3. ✖ πi
4. ✖ $-\pi i$

Question Number : 8 Question Id : 1051316128 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The inverse Laplace transform of $\frac{s+3}{s^2-4s+13}$ is

Options :

1. ✖ $e^{2t} [\cos 2t + 3 \sin 2t]$
2. ✔

$$\frac{e^{2t}}{3} [3 \cos 3t + 5 \sin 3t]$$

3. ✖ $e^{2t} [t + 3 \sin 3t]$

4. ✖ $\frac{e^{2t}}{5} [5 \cos 3t + 3 \sin 3t]$

Question Number : 9 Question Id : 1051316129 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Choose a possible probability density function from the given functions

Options :

1. ✖ $f(x) = \begin{cases} 1, & 0 \leq x \leq 2 \\ 0, & \text{otherwise} \end{cases}$

2. ✔ $f(x) = \begin{cases} e^{-x}, & x \geq 0 \\ 0, & x < 0 \end{cases}$

3. ✖ $f(x) = \begin{cases} \frac{6}{5}x(1+x), & x \geq 0 \\ 0, & x < 0 \end{cases}$

4. ✖ $f(x) = \begin{cases} x(1-x), & 0 \leq x \leq 1 \\ 0, & \text{elsewhere} \end{cases}$

Question Number : 10 Question Id : 1051316130 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The iterative formula for finding the approximate root of $f(x) = 0$ using Newton-Raphson method is

Options :

1. ✔

$$x_n = x_{n-1} - \frac{f(x_{n-1})}{f'(x_{n-1})}$$

2. ✖ $x_n = x_{n+1} + hf(x_n, y_n)$

3. ✖ $x_n = \frac{x_{n-1} + x_{n-2}}{f(x_{n-1})}$

4. ✖ $x_n = \frac{x_{n-1}f(x_{n-2}) - x_{n-2}f(x_{n-1})}{f(x_{n-1}) - f(x_{n-2})}$

Electrical Engineering

Section Id :	105131106
Section Number :	2
Section type :	Online
Mandatory or Optional :	Mandatory
Number of Questions :	110
Number of Questions to be attempted :	110
Section Marks :	110
Maximum Instruction Time :	0
Sub-Section Number :	1
Sub-Section Id :	105131106
Question Shuffling Allowed :	Yes

Question Number : 11 Question Id : 1051316131 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The work done by the force $F = 4a_x - 3a_y + 2a_z$ N in giving a 1nC charge a displacement of $10a_x + 2a_y - 7a_z$ m is

Options :

1. ✖ 103 nJ

2. ✔ 20 nJ

3. ✖ 64 nJ

4. ✖ 60 nJ

Question Number : 12 Question Id : 1051316132 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The superposition theorem is essentially based on the concept of

Options :

1. ✖ duality

2. ✖ reciprocity

3. ✖ non-linearity

4. ✔ linearity

Question Number : 13 Question Id : 1051316133 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

When both the number of turns and the core length of an inductive coil are doubled, its self-inductance will be

Options :

1. ✖ halved

2. ✖ unaffected

3. ✖ quadrupled

4. ✔ doubled

Question Number : 14 Question Id : 1051316134 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The magnetic susceptibility of diamagnetic materials is

Options :

1. ✖ Much more than zero
2. ✔ Less than zero
3. ✖ Equal to zero
4. ✖ Infinite

Question Number : 15 Question Id : 1051316135 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Two thin parallel wires carry currents along the same direction. The force experienced by one due to the other is

Options :

1. ✔ Perpendicular to the lines and attractive
2. ✖ Perpendicular to the lines and repulsive
3. ✖ Zero
4. ✖ Parallel to the lines

Question Number : 16 Question Id : 1051316136 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The surface integral of the normal component of electric flux density over any closed surface is equal to the following enclosed.

Options :

1. ✖ current
2. ✔ charge
3. ✖ voltage

4. ✖ power

Question Number : 17 Question Id : 1051316137 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Identify the statement that is not true for ferromagnetic material

Options :

1. ✖ They have large magnetic susceptibility
2. ✔ They have a fixed value of relative permeability
3. ✖ Energy loss is proportional to the area of the hysteresis loop
4. ✖ Above curie temperature, they lose their non-linearity property

Question Number : 18 Question Id : 1051316138 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The dipole moment per unit volume is known as

Options :

1. ✖ Dielectric constant
2. ✔ Polarization
3. ✖ Capacitance
4. ✖ Permittivity

Question Number : 19 Question Id : 1051316139 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

At resonance, voltage across L and C in series circuit is

Options :

1. ✓ equal and opposite
2. ✗ unity
3. ✗ infinite
4. ✗ zero

Question Number : 20 Question Id : 1051316140 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Choose the correct statement

Options :

- Capacitor behaves like a short circuit at very high frequency and inductor behaves like a
1. ✓ short circuit at very low frequency
- Capacitor behaves like an open circuit at very high frequency and inductor behaves like a
2. ✗ short circuit at very low frequency
- Capacitor behaves like a short circuit at very high frequency and inductor behaves like an
3. ✗ open circuit at very low frequency
- Capacitor behaves like an open circuit at very high frequency and inductor behaves like an
4. ✗ open circuit at very low frequency

Question Number : 21 Question Id : 1051316141 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

If all resistances in delta are equal to $30\ \Omega$, then each resistance in star is

Options :

1. ✗ $30\ \Omega$
2. ✗ $90\ \Omega$
3. ✓ $10\ \Omega$

4. ✖ 900 Ω

Question Number : 22 Question Id : 1051316142 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Phasor analysis is valid for

Options :

1. ✖ Transient signals
2. ✔ Steady state sinusoidal signals
3. ✖ Any type of signals
4. ✖ DC signals

Question Number : 23 Question Id : 1051316143 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Choose the correct statement

Options :

- The magnetic dipole moment is the sum of current and area of the loop, its direction is
1. ✖ normal to the loop
 2. ✖ The magnetic dipole moment is the product of current and area of the loop, it has no direction
- The magnetic dipole moment is the product of current and area of the loop, its direction is
3. ✔ normal to the loop
 4. ✖ The magnetic dipole moment is the sum of current and volume of the loop, its direction is normal to the loop

Question Number : 24 Question Id : 1051316144 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

At resonance, power factor in a parallel RLC circuit is

Options :

1. ✓ Unity
2. ✗ Zero
3. ✗ Infinite
4. ✗ 0.5

Question Number : 25 Question Id : 1051316145 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Thevenin equivalent of a circuit consists of

Options :

1. ✗ Current source and series resistance
2. ✗ Voltage source and series capacitance
3. ✓ Voltage source and series resistance
4. ✗ Current source and series capacitance

Question Number : 26 Question Id : 1051316146 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The varying electric fields are a source of

Options :

1. ✓ Displacement current
2. ✗ Conduction current
3. ✗ Convection current
4. ✗ Both conduction and convection current

Question Number : 27 Question Id : 1051316147 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Form factor of a sine wave is

Options :

1. ✖ 0.75

2. ✖ 0.65

3. ✖ 0.50

4. ✔ 1.11

Question Number : 28 Question Id : 1051316148 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Internal resistance of ideal current source is

Options :

1. ✖ Zero

2. ✔ Infinity

3. ✖ Unity

4. ✖ 100

Question Number : 29 Question Id : 1051316149 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The efficiency of a circuit at maximum power transfer condition is

Options :

1. ✖ 100%

2. ✔ 50%

3. ✖ 25%

4. ✖ 75%

Question Number : 30 Question Id : 1051316150 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

In a two wattmeter method, if one wattmeter reads negative then

Options :

1. ✖ Power factor > 0.5

2. ✖ Power factor $= 1$

3. ✔ Power factor < 0.5

4. ✖ Zero power factor

Question Number : 31 Question Id : 1051316151 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The copper and iron losses of a 1- ϕ transformer are equal at 90% of full load and its value is 162 W. The total loss at 80% of full load is

Options :

1. ✔ 145 W

2. ✖ 244 W

3. ✖ 128 W

4. ✖ 153 W

Question Number : 32 Question Id : 1051316152 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

In an ideal transformer, which of the following is correct?

Options :

1. ✖ $\left(\frac{V_1}{V_2}\right) = \left(\frac{I_1}{I_2}\right) = \left(\frac{N_1}{N_2}\right)$

2. ✖ $\left(\frac{V_1}{V_2}\right) = \left(\frac{I_2}{I_1}\right) = \left(\frac{N_2}{N_1}\right)$

3. ✔ $\left(\frac{V_1}{V_2}\right) = \left(\frac{I_2}{I_1}\right) = \left(\frac{N_1}{N_2}\right)$

4. ✖ $\left(\frac{V_2}{V_1}\right) = \left(\frac{I_1}{I_2}\right) = \left(\frac{N_1}{N_2}\right)$

Question Number : 33 Question Id : 1051316153 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

In delta-star connection, the phase displacement between the primary voltage and secondary emfs is

Options :

1. ✔ 30°

2. ✖ -60°

3. ✖ 60°

4. ✖ -30°

Question Number : 34 Question Id : 1051316154 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A transformer has full load copper loss of 400 W. The copper loss at half full load will be

Options :

1. ✖ 400 W
2. ✖ 200 W
3. ✖ 300 W
4. ✔ 100 W

Question Number : 35 Question Id : 1051316155 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The load current of a step down 250/200 V auto-transformer is 100 A. The conductive and inductive powers transformed are

Options :

1. ✖ 4 kVA and 20 kVA
2. ✖ 4 kVA and 16 kVA
3. ✔ 16 kVA and 4 kVA
4. ✖ 20 kVA and 4 kVA

Question Number : 36 Question Id : 1051316156 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The eddy current loss and hysteresis loss of 1- ϕ , 100 kVA, 50 Hz transformer are 4 kW and 6 kW respectively. If frequency is increased by 10%, then total loss is

Options :

1. ✔ 11.44 kW
2. ✖ 11.66 kW
3. ✖ 11.00 kW
4. ✖ 12.10 kW

Question Number : 37 Question Id : 1051316157 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

In a wave winding, if y_b and y_c are back and commutator pitches respectively, then the front pitch y_f is given by

Options :

1. ✖ $y_f = 2y_b + y_c$

2. ✔ $y_f = 2y_c - y_b$

3. ✖ $y_f = 2y_b - y_c$

4. ✖ $y_f = 2y_c + y_b$

Question Number : 38 Question Id : 1051316158 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A DC generator with 8-pole, 480 armature conductors, wave winding, draws an armature current of 200 A. When brushes are shifted by 6° electrical from GNP, the cross-magnetising amp-turn/pole is

Options :

1. ✖ 2200

2. ✖ 200

3. ✖ 800

4. ✔ 2800

Question Number : 39 Question Id : 1051316159 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

To control voltage of a long shunt dc compound generator, a diverter resistance is connected across

Options :

1. ✖ shunt and series field windings
2. ✔ series field winding
3. ✖ shunt field winding
4. ✖ series field and armature winding

Question Number : 40 Question Id : 1051316160 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

When load current of a dc series motor is increased, then

Options :

1. ✔ speed decreases non-linearly and torque increases non-linearly
2. ✖ flux increases non-linearly and torque increases linearly
3. ✖ speed decreases linearly and torque increases non-linearly
4. ✖ flux increases linearly and torque increases non-linearly

Question Number : 41 Question Id : 1051316161 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The disadvantage of Hopkinson's test on two dc shunt machines is

Options :

1. ✖ copper and iron losses are assumed equal
2. ✖ requires two unidentical machines
3. ✔ iron and mechanical losses are assumed equal
4. ✖ iron and mechanical losses are assumed unequal

Question Number : 42 Question Id : 1051316162 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Slope of the tangent drawn on initial portion of O.C.C of synchronous generator is

Options :

1. ✖ Unsaturated synchronous resistance
2. ✖ Saturated synchronous impedance
3. ✖ Critical resistance
4. ✔ Unsaturated synchronous impedance

Question Number : 43 Question Id : 1051316163 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

If the locus of minimum armature currents of V-curves of synchronous motor is a straight line, then the slope of the line is

Options :

1. ✔ positive
2. ✖ negative
3. ✖ zero
4. ✖ infinite

Question Number : 44 Question Id : 1051316164 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

If δ is load angle, the real power of 3- ϕ synchronous motor is

Options :

1. ✖ directly proportional to δ
2. ✔

directly proportional to $\sin\delta$

3. ✖ inversely proportional to $\sin\delta$

4. ✖ inversely proportional to δ

Question Number : 45 Question Id : 1051316165 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Speed of a 3- ϕ , 4-pole, 60 Hz induction motor at 75% of full-load is 1700 rpm. The speed at full-load can be

Options :

1. ✖ 1750 rpm

2. ✖ 1800 rpm

3. ✖ 1700 rpm

4. ✔ 1600 rpm

Question Number : 46 Question Id : 1051316166 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Frequency of rotor current of a 3- ϕ , 4-pole, 50 Hz induction motor is 3 Hz. Speed of the motor is

Options :

1. ✖ 1425 rpm

2. ✖ 1497 rpm

3. ✖ 1455 rpm

4. ✔ 1410 rpm

Question Number : 47 Question Id : 1051316167 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

When the supply voltage to an induction motor is reduced by 10%, the maximum torque will be decreased approximately by

Options :

1. ✖ 5%
2. ✖ 10%
3. ✖ 20%
4. ✔ 40%

Question Number : 48 Question Id : 1051316168 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Two 3- ϕ induction motors with p_1 and p_2 poles are cascaded together. Then the possible number of speeds are

Options :

1. ✖ two
2. ✖ one
3. ✔ four
4. ✖ three

Question Number : 49 Question Id : 1051316169 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

In torque-slip curve of a 1- ϕ induction motor, the backward torque is

Options :

1. ✖ negative from slip $s=0$ to $s=1$ and positive from slip $s=1$ to $s=2$
2. ✔ negative from slip $s=0$ to $s=2$

3. ✖ negative from slip $s=0.5$ to $s=1.5$
4. ✖ negative from slip $s=1$ to $s=2$ and positive from slip $s=0$ to $s=1$

Question Number : 50 Question Id : 1051316170 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The step angle of a 3- ϕ (A, B, C), 6 stator pole, 4 rotor teeth stepper motor if excited sequentially i.e, A, AB, B, BC, C, CA, and so on is

Options :

1. ✖ 3.75°
2. ✖ 30°
3. ✔ 15°
4. ✖ 7.5°

Question Number : 51 Question Id : 1051316171 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

What is the VA output required for a CT of 5 A rated secondary current when burden consists of a relay requiring 7.5 VA at 5 A and connecting lead resistance of 0.08 ohm?

Options :

1. ✖ 7.5 VA
2. ✖ 15.0 VA
3. ✔ 9.5 VA
4. ✖ 1.3 VA

Question Number : 52 Question Id : 1051316172 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

In which relay, the relay operation depends upon the ratio of voltage to current?

Options :

1. ✗ directional
2. ✗ differential
3. ✓ distance
4. ✗ reverse

Question Number : 53 Question Id : 1051316173 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Resistance switching is used in circuit breaker to

Options :

1. ✗ decrease the restriking voltage and increase the severity of transient oscillations
2. ✗ increase the severity of transient oscillations and the severity of transients
3. ✓ Reduce the restriking voltage and severity of transient oscillations
4. ✗ increase the restriking voltage and reducing the severity of transient oscillations

Question Number : 54 Question Id : 1051316174 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

For an n^{th} order system to be state controllable, which of the following is not a correct statement?

Options :

1. ✗ The controllability matrix must be of rank n
2. ✗ The controllability matrix must contain n linearly independent column vectors
3. ✓ The controllability matrix must contain n linearly dependent column vectors

4. ✖ The determinant of controllability matrix is not singular

Question Number : 55 Question Id : 1051316175 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A generating station has a maximum demand of 25 MW, a load factor of 60%, a plant capacity factor of 50 %. What is the reserve capacity of the plant?

Options :

1. ✖ 25 MW

2. ✖ 15 MW

3. ✖ 7.5 MW

4. ✔ 5 MW

Question Number : 56 Question Id : 1051316176 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The current densities in human bodies lie in the proximity of the transmission line are

Options :

1. ✖ induced by electric fields are much lower than those induced by magnetic fields

2. ✖ induced by electric fields only

3. ✔ induced by electric fields are much higher than those induced by magnetic fields

4. ✖ induced by magnetic field only

Question Number : 57 Question Id : 1051316177 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The characteristics of rate of convergence of Gauss -Siedel method and Newton Raphson method respectively are

Options :

1. ✖ linear, linear
2. ✖ quadratic, quadratic
3. ✖ quadratic, linear
4. ✔ linear, quadratic

Question Number : 58 Question Id : 1051316178 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

In case of the compensation of the power transmission lines, for the same voltage boost, the reactive power capacity of a shunt capacitor is _____ that of a series capacitor

Options :

1. ✖ equal to
2. ✔ greater than
3. ✖ lesser than
4. ✖ 0.0001 times

Question Number : 59 Question Id : 1051316179 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Under steady state short circuit conditions, the armature reaction of a synchronous generator is

Options :

1. ✖ Cross-magnetizing
2. ✔ Demagnetizing

- 3. ✖ Magnetizing
- 4. ✖ Partially cross-magnetizing

Question Number : 60 Question Id : 1051316180 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A fully transposed transmission line has

Options :

- 1. ✔ Zero sequence impedance larger than the positive sequence impedance
- 2. ✖ Zero sequence impedance smaller than the positive sequence impedance
- 3. ✖ Zero sequence impedance equal to positive sequence impedance
- 4. ✖ Positive sequence impedance is larger than the negative sequence impedance

Question Number : 61 Question Id : 1051316181 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The swing equation of a synchronous generator is

Options :

- 1. ✖ Linear, second order differential equation
- 2. ✔ Non-linear, second order differential equation
- 3. ✖ Non-linear, second order algebraic equation
- 4. ✖ Non-linear, first order differential equation

Question Number : 62 Question Id : 1051316182 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

In nuclear reactors, the most commonly used neutron absorber is

Options :

1. ✖ Uranium
2. ✖ Hydrogen
3. ✔ Boron
4. ✖ Oxygen

Question Number : 63 Question Id : 1051316183 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The insulation resistance of a single core cable is $160 \text{ M}\Omega/\text{km}$. The insulation resistance for 4 km length is

Options :

1. ✖ $640 \text{ M}\Omega$
2. ✖ $160 \text{ M}\Omega$
3. ✔ $40 \text{ M}\Omega$
4. ✖ $80 \text{ M}\Omega$

Question Number : 64 Question Id : 1051316184 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The insulators used in transmission lines at river and road crossing are

Options :

1. ✔ Strain type
2. ✖ Suspension type
3. ✖ Pin type
4. ✖ Cup type

Question Number : 65 Question Id : 1051316185 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The effect of increase in temperature on transmission lines

Options :

1. ✖ Sag and tension of conductor decreases
2. ✖ Sag and tension of conductor increases
3. ✔ Sag increases and tension of the conductor decreases
4. ✖ Sag decreases and tension of the conductor increases

Question Number : 66 Question Id : 1051316186 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

In distribution systems, the size of conductor is determined by using

Options :

1. ✖ Faraday's law
2. ✔ Kelvin's law
3. ✖ Ohm's law
4. ✖ Kirchhoff's law

Question Number : 67 Question Id : 1051316187 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Bonding of the cable is done to

Options :

1. ✖ Decrease the effective R and L
2. ✖ Increase the effective R and L

3. ✖ Decrease the effective R but increase L
4. ✔ Increase the effective R but reduce L

Question Number : 68 Question Id : 1051316188 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The most frequently occurred fault in the power system is

Options :

1. ✖ L-L-G
2. ✖ L-L
3. ✖ L-L-L
4. ✔ L-G

Question Number : 69 Question Id : 1051316189 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The transfer function model of a system is the reshaping of the differential equations of which type of system?

Options :

1. ✖ linear time varying
2. ✔ linear time invariant
3. ✖ non-linear time invariant
4. ✖ non-linear time varying

Question Number : 70 Question Id : 1051316190 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The per unit value of a $2\ \Omega$ resistor at 100 MVA base and 10 kV base voltage is

Options :

1. ✓ 2
2. ✗ 4
3. ✗ 0.5
4. ✗ 0.2

Question Number : 71 Question Id : 1051316191 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Match the following electrical system with mechanical system based on current-force analogy

Electrical System		Mechanical system	
A	Voltage	I	displacement
B	flux linkages	II	Moment of inertia
C	capacitance	III	torque
		IV	angular velocity

Options :

1. ✓ A – IV, B – I, C – II
2. ✗ A – I, B – II, C – III
3. ✗ A – III, B – IV, C – II
4. ✗ A – II, B – I, C – IV

Question Number : 72 Question Id : 1051316192 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Compared with an induction motor, AC servo motor speed-torque characteristics and X/R ratio respectively are

Options :

1. ✗ nearly linear, large

- 2. ✖ more non-linear, large
- 3. ✔ nearly linear, small
- 4. ✖ more non-linear, small

Question Number : 73 Question Id : 1051316193 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The steady-state error of Type-2 system for a standard unit velocity input is

Options :

- 1. ✖ $\frac{1}{(1+K_v)}$
- 2. ✖ ∞
- 3. ✖ $\frac{1}{K_v}$
- 4. ✔ 0

Question Number : 74 Question Id : 1051316194 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The centroid of the following system is

$$G(s)H(s) = \frac{K(s+10)(s+20)}{s^3(s+100)(s+800)}$$

Options :

- 1. ✖ 290
- 2. ✔ -290
- 3. ✖ 310
- 4. ✖ -310

Question Number : 75 Question Id : 1051316195 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

For the following system, the angles of asymptotes are

$$G(s)H(s) = \frac{K}{s(s^2 + 2s + 1)}$$

Options :

1. ✖ $45^\circ, 135^\circ, 225^\circ$
2. ✖ $60^\circ, 120^\circ, 180^\circ$
3. ✔ $60^\circ, 180^\circ, 300^\circ$
4. ✖ $60^\circ, 150^\circ, 240^\circ$

Question Number : 76 Question Id : 1051316196 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Natural frequency of oscillations of the following transfer function is

$$\frac{C(s)}{R(s)} = \frac{1}{(s^2 + 0.5s + 1)}$$


Options :

1. ✖ $\omega_n = 0.5$
2. ✖ $\omega_n = 2$
3. ✖ $\omega_n = 0.25$
4. ✔ $\omega_n = 1$

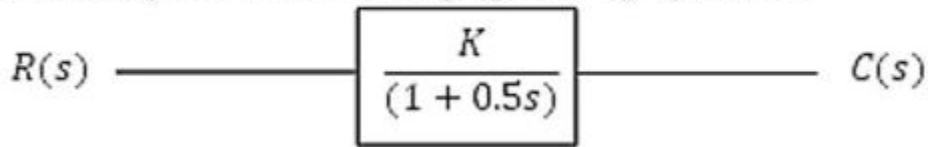Question Number : 77 Question Id : 1051316197 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Sensitivity of the following open loop system is



Options :

1. ✓ 1
2. ✗ 2/3
3. ✗ 0.5
4. ✗ 3/2

Question Number : 78 Question Id : 1051316198 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Which of the following pair of electro-mechanical devices are part of Synchro?

Options :

1. ✗ AC tacho generator and Transmitter
2. ✓ Transmitter and Control transformer
3. ✗ Control transformer and Receiver
4. ✗ Receiver and AC tacho generator

Question Number : 79 Question Id : 1051316199 Question Type : MCQ Option Shuffling : Yes
Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Choose the correct statement with reference to standard test signals

Options :

1. ✗ Unit impulse signal is obtained by integrating unit step signal
2. ✗ Unit step signal is obtained by differentiating unit impulse signal
3. ✗ Unit ramp signal is obtained by differentiating unit step signal

4. ✓ Unit parabolic signal is obtained by integrating unit ramp signal

Question Number : 80 Question Id : 1051316200 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Time constant of a first order unit step input system is defined as the time at which unit step response reaches

Options :

1. ✓ 63.2% of steady state value
2. ✗ 66.7% of steady state value
3. ✗ 36.8% of steady state value
4. ✗ 33.3% of steady state value

Question Number : 81 Question Id : 1051316201 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Steady-state error of the following second order system for a unit ramp input is

$$\frac{C(s)}{R(s)} = \frac{\omega_n^2}{(s^2 + 2\delta\omega_n s + \omega_n^2)}$$

Options :

1. ✗ $\frac{\delta}{2\omega_n}$
2. ✓ $\frac{2\delta}{\omega_n}$
3. ✗ $\frac{2\delta}{\omega_n^2}$
4. ✗

$$\frac{\delta}{2\omega_n^2}$$

Question Number : 82 Question Id : 1051316202 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

For the given open loop system, the poles of unity feed-back closed loop system are

$$G(s) = \frac{1}{(s+2)(s+4)}$$

Options :

1. ✖ - 3, 3
2. ✖ - 1, - 3
3. ✔ - 3, - 3
4. ✖ 1, 3

Question Number : 83 Question Id : 1051316203 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Feeding the distributor at more than one point

Options :

1. ✔ reduces the power loss in the distributor
2. ✖ reduces the efficiency of the distributor
3. ✖ increases the power loss in the distributor
4. ✖ increases the total voltage drop in the distributor

Question Number : 84 Question Id : 1051316204 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The state equation of a dynamical system is: $\dot{X} = AX + Bu$, where $[A]$ is a 3×3 system matrix and $[B]$ is a 3×1 input matrix. Then the controllability matrix Q_c is

Options :

1. ✓ $Q_c = [B \mid AB \mid A^2B]$
2. ✗ $Q_c = [A \mid AB \mid A^2B]$
3. ✗ $Q_c = [B \mid AB \mid B^2A]$
4. ✗ $Q_c = [A \mid AB \mid B^2A]$

Question Number : 85 Question Id : 1051316205 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

If transfer function of a controller is given by: $G_c(s) = \frac{(K_1s^2 + K_2s + K_3)}{s}$, then the proportional, integral and derivative constants are

Options :

1. ✗ K_1, K_2 and K_3 respectively
2. ✗ K_3, K_2 and K_1 respectively
3. ✗ K_2, K_1 and K_3 respectively
4. ✓ K_2, K_3 and K_1 respectively

Question Number : 86 Question Id : 1051316206 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Which of the following bridge is not used for the measurement of capacitance?

Options :

1. ✗ Schering bridge

2. ✖ Wein's bridge
3. ✖ De Sauty's bridge
4. ✔ Hay's bridge

Question Number : 87 Question Id : 1051316207 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

An energy meter makes 600 revolutions per kWh. If it makes 300 revolutions in 30 minutes, then the load power is

Options :

1. ✖ 0.5 kW
2. ✔ 1 kW
3. ✖ 2 kW
4. ✖ 3 kW

Question Number : 88 Question Id : 1051316208 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Resolution of a $3\frac{1}{2}$ digit DVM is

Options :

1. ✖ $\frac{1}{100}$
2. ✖ $\frac{1}{1000}$
3. ✔ $\frac{1}{2000}$
4. ✖ $\frac{1}{10000}$

Question Number : 89 Question Id : 1051316209 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A DC potentiometer has a potential gradient of 20 mV/cm. The balancing lengths for a standard cell and an unknown voltage are 75 cm and 120 cm respectively. If the standard cell voltage is 1.50 V, then the unknown voltage is

Options :

1. ✖ 1.80 V
2. ✖ 2.00 V
3. ✔ 2.40 V
4. ✖ 3.20 V

Question Number : 90 Question Id : 1051316210 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A PMMC instrument has full-scale deflection current of 50 μ A and coil resistance of 1 k Ω . The resistance to be added in series to convert it into 10 V voltmeter is

Options :

1. ✖ 99 k Ω
2. ✔ 199 k Ω
3. ✖ 9 k Ω
4. ✖ 1 M Ω

Question Number : 91 Question Id : 1051316211 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A moving-iron voltmeter reads correctly on DC. If connected to a 50 Hz sinusoidal AC source whose RMS value equals the DC value, then the reading will be

Options :

1. ✖ greater than the DC reading
2. ✖ less than the DC reading
3. ✔ same as the DC reading
4. ✖ zero

Question Number : 92 Question Id : 1051316212 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A current transformer has ratio 500/5. If the burden is 2 VA at rated secondary current, the corresponding burden impedance is

Options :

1. ✔ 0.08 Ω
2. ✖ 0.4 Ω
3. ✖ 0.8 Ω
4. ✖ 2.0 Ω

Question Number : 93 Question Id : 1051316213 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A digital frequency meter counts 5000 pulses during a gate time of 0.1 s. The measured frequency is

Options :

1. ✖ 500 Hz
2. ✖ 5 kHz
3. ✔ 50 kHz
4. ✖ 500 kHz

Question Number : 94 Question Id : 1051316214 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

An analog instrument has a specified accuracy of $\pm 1\%$ of full-scale reading. If its full-scale value is 300 V and it reads 120 V, the maximum percentage error with respect to the indicated reading is

Options :

1. ✖ 1%
2. ✖ 1.5%
3. ✔ 2.5%
4. ✖ 5%

Question Number : 95 Question Id : 1051316215 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A strain gauge has gauge factor 2.1 and nominal resistance 120 Ω . If it is subjected to a strain of 1000 $\mu\epsilon$, the change in resistance is

Options :

1. ✖ 0.126 Ω
2. ✔ 0.252 Ω
3. ✖ 0.504 Ω
4. ✖ 1.20 Ω

Question Number : 96 Question Id : 1051316216 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A silicon diode has a reverse saturation current of 10^{-12} A at 300 K. The approximate increase in temperature such that saturation current doubles is

Options :

1. ✖ 5°C
2. ✔ 10°C
3. ✖ 15°C
4. ✖ 20°C

Question Number : 97 Question Id : 1051316217 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A BJT in CE mode has $\beta=120$ and collector current $I_C=2.4\text{ mA}$. The small-signal transconductance at room temperature ($V_T \approx 25\text{ mV}$) is approximately

Options :

1. ✖ 0.024 S
2. ✖ 0.048 S
3. ✔ 0.096 S
4. ✖ 0.12 S

Question Number : 98 Question Id : 1051316218 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The transconductance of MOSFET in saturation is

Options :

1. ✖ $k(V_{GS}-V_T)$
2. ✔ $2k(V_{GS}-V_T)$
3. ✖ kV_{DS}
4. ✖ Constant

Question Number : 99 Question Id : 1051316219 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A phase shift oscillator requires minimum gain of

Options :

1. ✖ 1
2. ✖ 10
3. ✔ 29
4. ✖ 100

Question Number : 100 Question Id : 1051316220 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

An op-amp with slew rate $0.5 \text{ V}/\mu\text{s}$ is used to generate a sine wave of amplitude 10 V.

Maximum frequency without distortion is approximately

Options :

1. ✔ 8 kHz
2. ✖ 16 kHz
3. ✖ 32 kHz
4. ✖ 50 kHz

Question Number : 101 Question Id : 1051316221 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A first-order high-pass RC filter has cutoff frequency $f_c = 1 \text{ kHz}$. If the magnitude of the transfer function is measured at $f = 500 \text{ Hz}$, the gain magnitude is

Options :

1. ✖ 0.25
2. ✔ 0.45

3. ✖ 0.71

4. ✖ 0.89

Question Number : 102 Question Id : 1051316222 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A synchronous 3-bit binary counter is currently in state $Q_2Q_1Q_0=101$. After two clock pulses, its state will be

Options :

1. ✔ 111

2. ✖ 000

3. ✖ 001

4. ✖ 010

Question Number : 103 Question Id : 1051316223 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A 4-variable Boolean function is implemented using an 8:1 multiplexer. Three variables are used as select lines, and the remaining variable is connected appropriately to the data inputs. The minimum number of 8:1 multiplexers required to realize any arbitrary 4-variable Boolean function is

Options :

1. ✔ 1

2. ✖ 2

3. ✖ 4

4. ✖ 8

Question Number : 104 Question Id : 1051316224 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Resolution of an 8-bit ADC with 5V reference is

Options :

1. ✖ 5 V
2. ✖ 2.5 V
3. ✔ 19.5 mV
4. ✖ 39 mV

Question Number : 105 Question Id : 1051316225 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

An 8085 microprocessor executes an instruction in 4 machine cycles containing 4, 3, 3, and 3 T-states respectively. If the clock frequency is 3 MHz, the execution time is approximately

Options :

1. ✖ 3.33 μ s
2. ✔ 4.33 μ s
3. ✖ 4.67 μ s
4. ✖ 13.33 μ s

Question Number : 106 Question Id : 1051316226 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The slip of a 3- ϕ , 50 Hz, induction motor fed by 3- ϕ , 50 Hz inverter is 's' at fundamental frequency. At 5th harmonic frequency, the harmonic slip is nearly equal to

Options :

1. ✖ 5s
2. ✖ $\frac{s}{5}$

3. ✓ 1.2

4. ✗ 1

Question Number : 107 Question Id : 1051316227 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A 3- ϕ , 50 Hz synchronous motor is to be operated at constant flux by frequency control. If frequency is decreased by 4% of rated frequency at the same flux, then the voltage should be

Options :

1. ✓ Decreased by 4%

2. ✗ Increased by 4%

3. ✗ Neither increased nor decreased

4. ✗ Increased by 4.5%

Question Number : 108 Question Id : 1051316228 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A power diode is open circuited, and a reverse dc voltage is applied to get a faster turn-off time. During reverse recovery time

- (a) When current is negative peak, voltage is zero
- (b) When voltage is negative peak, current is zero
- (c) When current is negative peak, voltage is not zero
- (d) When voltage is negative peak, current is not zero

Choose the correct answer

Options :

1. ✗ (a) true, (c) true and (d) true

2. ✗ (b) true, (c) true and (d) false

3. ✗ (b) false, (c) false and (d) true

4. ✓ (a) true, (c) false and (d) true

Question Number : 109 Question Id : 1051316229 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

Power MOSFETs are extremely popular in

Options :

1. ✓ Low voltage, low power and high frequency applications
2. ✗ Low voltage, high power and high frequency applications
3. ✗ High voltage, high power and low frequency applications
4. ✗ High voltage, low power and low frequency applications

Question Number : 110 Question Id : 1051316230 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

In IGBT an improved Miller feedback effect is seen (compared with MOSFET) because, ratio of gate-collector capacitance to gate-emitter capacitance is

Options :

1. ✗ Unity
2. ✓ Lower
3. ✗ Higher
4. ✗ Very large

Question Number : 111 Question Id : 1051316231 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

In the first quadrant of V-I characteristics of Uni-Junction Transistor, the slopes of characteristic are in the following sequence

Options :

1. ✖ Negative, zero, positive, zero and negative
2. ✔ Positive, zero, negative, zero and positive
3. ✖ Positive, zero, negative, zero and negative
4. ✖ Negative, zero, positive, zero and positive

Question Number : 112 Question Id : 1051316232 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The triggering pulses for 1- ϕ , full wave converter using Zero Crossing Detector, pulse amplifier and gate pulse isolation transformer, are obtained during

Options :

1. ✖ Ramp voltage with negative slope is less than control dc voltage
2. ✖ Ramp voltage with negative slope is more than control dc voltage
3. ✔ Ramp voltage with positive slope is more than control dc voltage
4. ✖ Ramp voltage with positive slope is less than control dc voltage

Question Number : 113 Question Id : 1051316233 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A 3- ϕ semi-converter with R-L load consists of _____ diodes and operates in _____

Options :

1. ✖ 4, four quadrants
2. ✖ 3, four quadrants

3. ✖ 4, one quadrant

4. ✔ 3, one quadrant

Question Number : 114 Question Id : 1051316234 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

A 3- ϕ fully controlled converter can be operated as a semi-converter, if

- (a) One of the input ac supplies is disconnected and the thyristors connected to it are triggered at 180 degrees.
- (b) One of the input ac supplies is disconnected and the thyristors connected to it are triggered at zero degrees.
- (c) A free-wheeling diode can be connected across the load in the same direction of thyristors
- (d) A free-wheeling diode can be connected across the load in the opposite direction of thyristors

Choose the correct answer

Options :

1. ✖ (a) and (c) are false

2. ✖ (b) and (d) are false

3. ✔ (b) and (c) are true

4. ✖ (d) and (a) are true

Question Number : 115 Question Id : 1051316235 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The input dc voltage of a 1- ϕ full bridge inverter is 141.4 V and its duty ratio is 0.49. Then its approximate average and rms voltages are

Options :

1. ✖ 69.3 V and 202 V respectively

2. ✖ 99 V and 202 V respectively

3. ✓ 69.3 V and 99 V respectively

4. ✗ 99 V and 69.3 V respectively

Question Number : 116 Question Id : 1051316236 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The fundamental frequency and peak voltage of an inverter are f and V_m respectively. When it contains all odd harmonics, then its frequency and rms voltage of 5th harmonic are

Options :

1. ✗ $5f$ and $\frac{5V_m}{\sqrt{2}}$ respectively

2. ✗ $\frac{f}{5}$ and $\frac{V_m}{5}$ respectively

3. ✗ $\frac{f}{5}$ and $\frac{V_m}{5\sqrt{2}}$ respectively

4. ✓ $5f$ and $\frac{V_m}{5\sqrt{2}}$ respectively

Question Number : 117 Question Id : 1051316237 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

If α is ratio $\frac{T_{ON}}{T}$ of chopper, then the ratio of input voltage to output voltage of step down and step-up chopper respectively are

Options :

1. ✓ $\frac{1}{\alpha}$ and $(1-\alpha)$

2. ✗ $\frac{1}{\alpha}$ and $\frac{1}{(1-\alpha)}$

3. ✖ α and $(1-\alpha)$

4. ✖ α and $\frac{1}{(1-\alpha)}$

Question Number : 118 Question Id : 1051316238 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

For a step-down Type A chopper, the waveforms of input current I and output current I_o respectively are

Options :

- 1. ✖ discontinuous and continuous for a resistive load
- 2. ✔ discontinuous and discontinuous for a resistive load
- 3. ✖ continuous and continuous for an inductive load
- 4. ✖ continuous and discontinuous for an inductive load

Question Number : 119 Question Id : 1051316239 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes

Correct Marks : 1 Wrong Marks : 0

The number of pulses per half cycle of PWM inverter is changed, then

Options :

- 1. ✖ The rms output voltage does not change, but the frequency changes
- 2. ✖ Both rms output voltage and output frequency do not change
- 3. ✔ The rms output voltage changes, but the frequency does not change
- 4. ✖ Both rms output voltage and output frequency change

Question Number : 120 Question Id : 1051316240 Question Type : MCQ Option Shuffling : Yes

Display Question Number : Yes**Correct Marks : 1 Wrong Marks : 0**

A dc motor is connected to a 214 V rms (L-L), 3- ϕ , 50 Hz line using a 3- ϕ bridge converter. If the firing angle is $\frac{\pi}{6}$, full load armature current is 2500 A and armature resistance is 4 m Ω , then the back emf is

Options :

1. ✖ 204 V
2. ✖ 260.3 V
3. ✖ 250.3 V
4. ✔ 240.3 V

prepp
Your Personal Exam Guide